

# Electronic Technology Design and Workshop

Presented and updated by

**Przemek Sekalski**

DMCS room 2

2007




# Electronic Technology Design and Workshop

## Lecture 4

### Microelectronics - elementary gates



# ETDW course road map

- ✓ Schematic edition, libraries of elements
  - ✓ Circuit simulation & netlist generation
  - ✓ **Microelectronics - full custom design and simulation**
  - ✓ Microelectronics - simple layout synthesis
  - ✓ Hardware description languages - behavioural description
  - ✓ Logic & sequential synthesis - programmable logic devices
  - ✓ PCB design – auto-routing
-  Project - bringing the pieces together




# Outline

- **Inverter (NOT)**
- **NAND**
- **NOR**
- **Transmission gate**
- **XOR**
- **Ring oscillator**




# CMOS inverter cross-section

 


Note that the PMOS transistor is formed in a separate  $n$ -type region, known as an  $n$  well. Another arrangement is also possible in which an  $n$ -type body is used and the  $n$  device is formed in a  $p$  well.

# CMOS inverter scheme

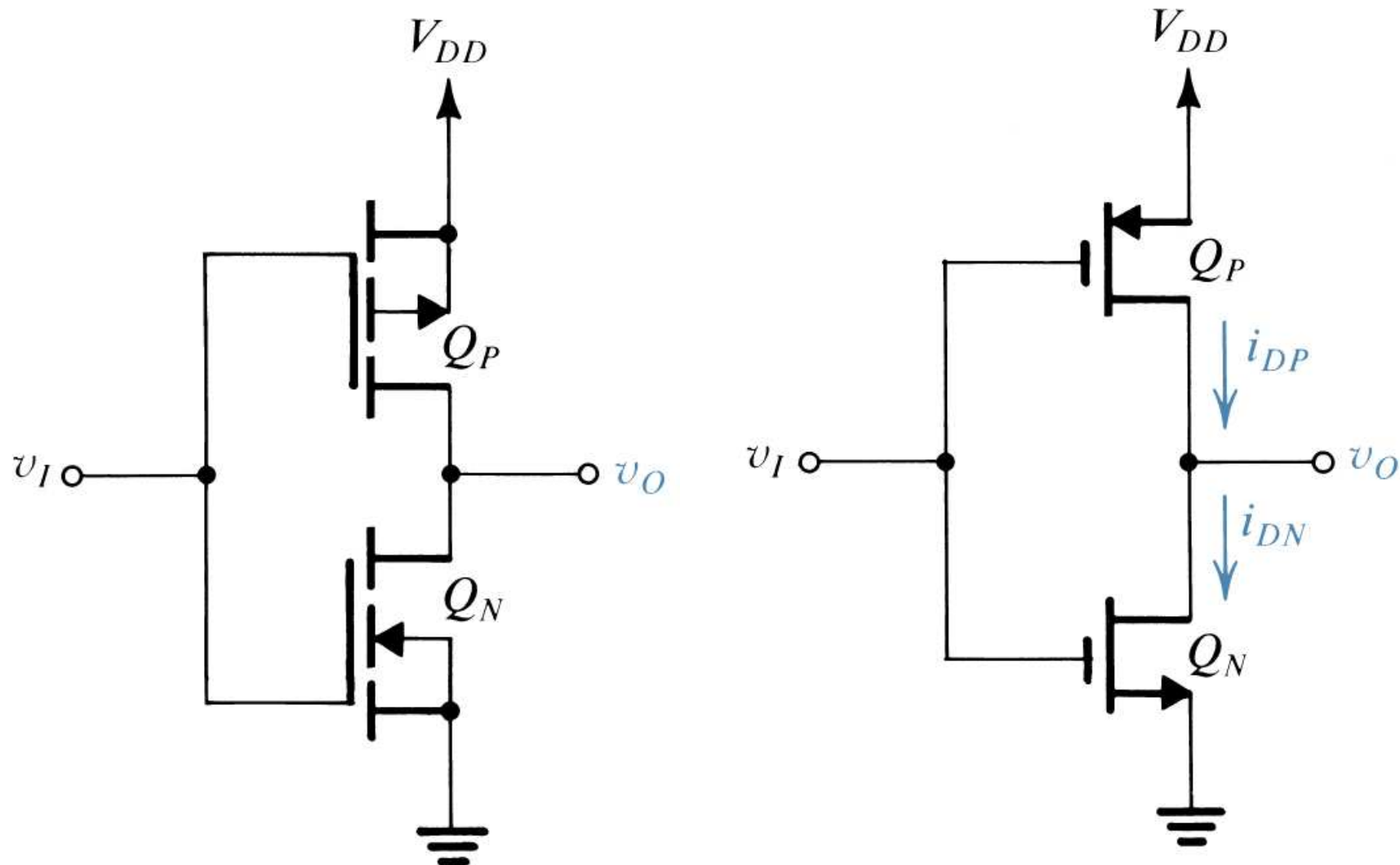



# CMOS inverter and pair of switches

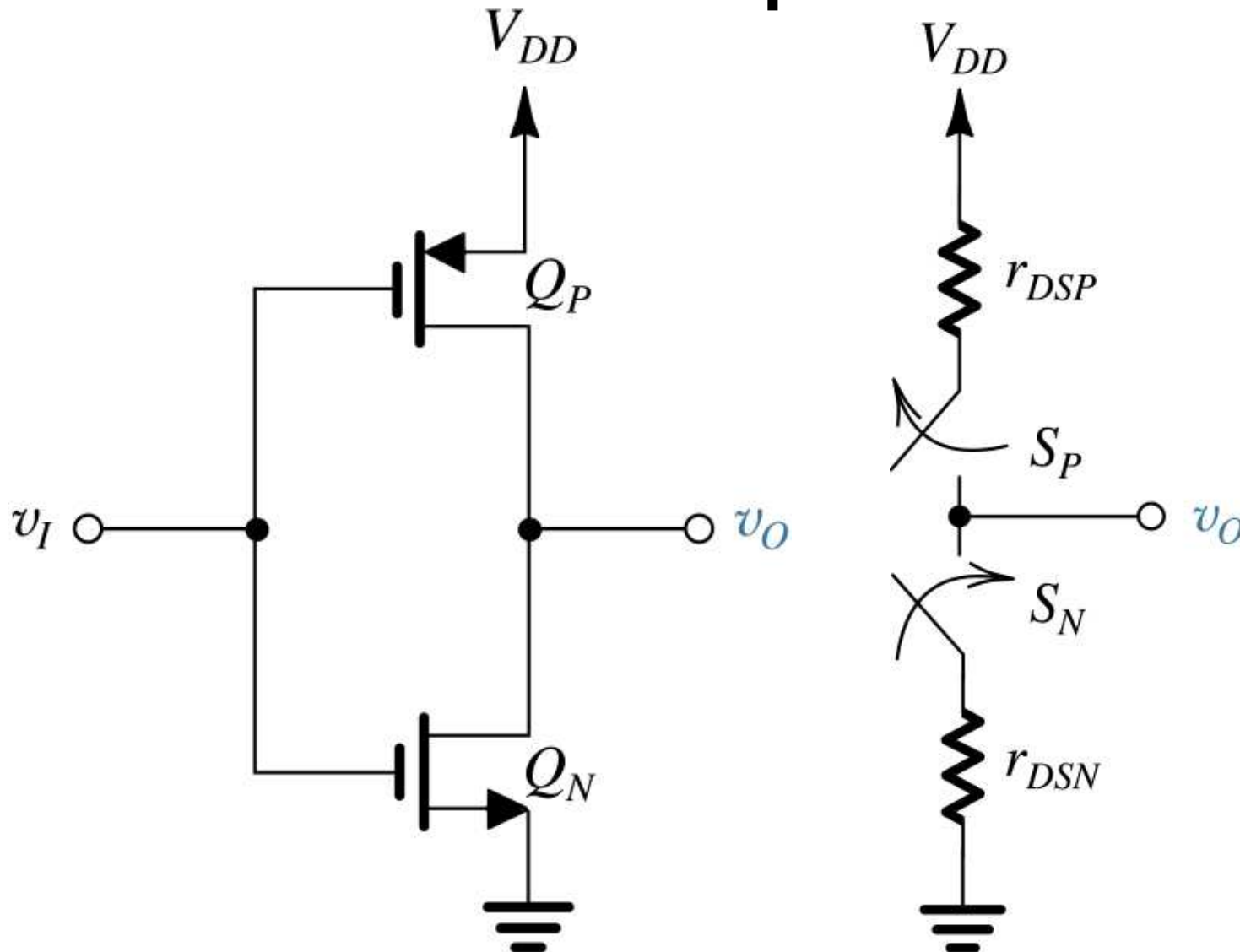


**Note:** switches must operate in a complementary fashion.

# CMOS inverter operation

$v_1$  is high

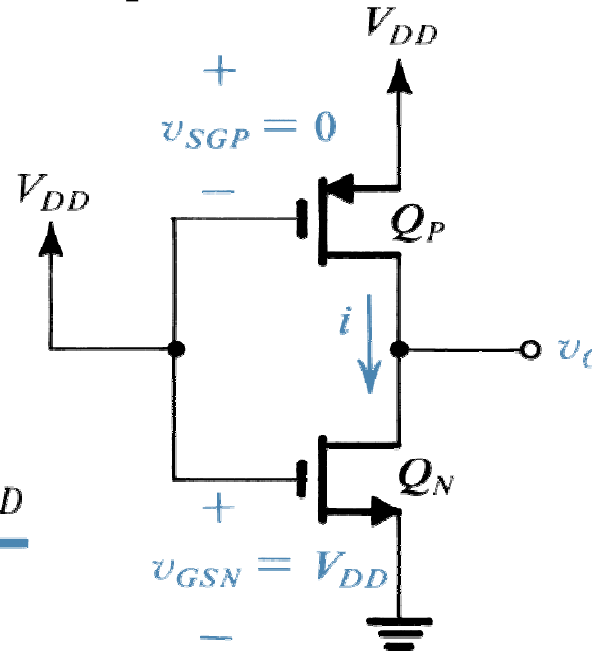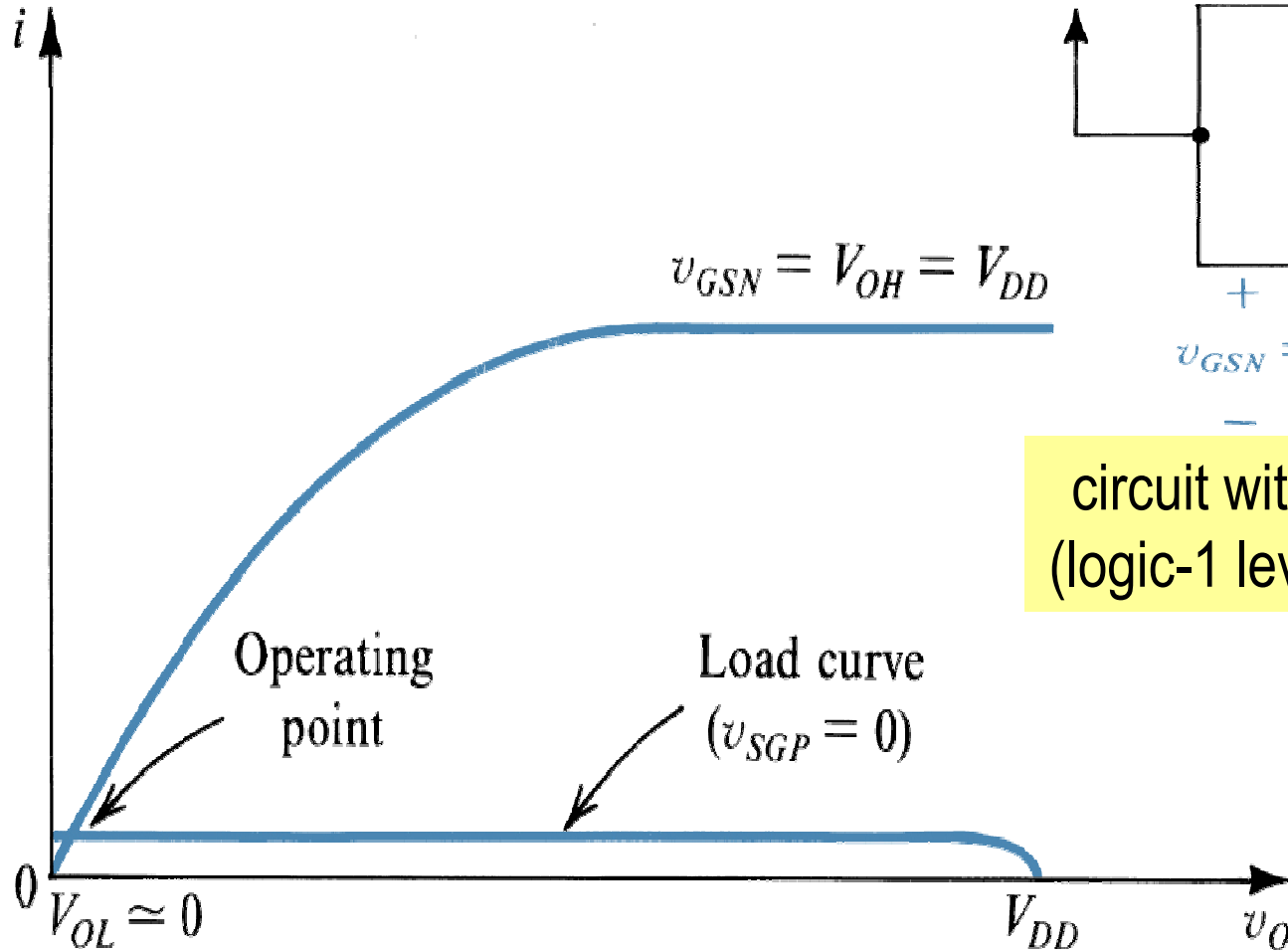

 circuit with  $v_1 = V_{DD}$   
(logic-1 level, or  $V_{OH}$ );





equivalent circuit.

graphical construction to determine the operating point




# CMOS inverter operation

$v_1$  is low

  

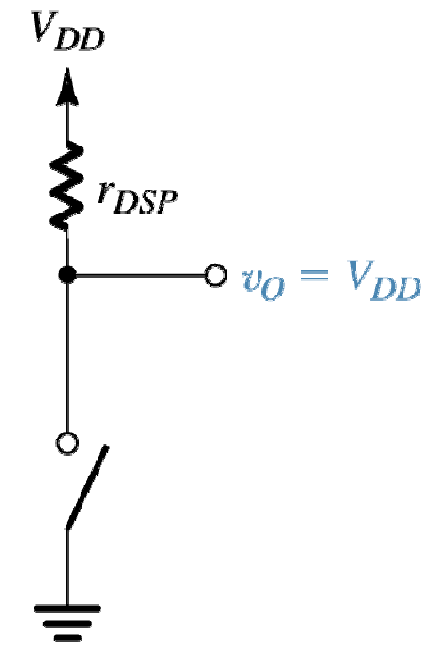
circuit with  $v_1 = 0V$   
(logic-0 level, or  $V_{OL}$ );





equivalent circuit.

graphical construction to determine the operating point
 
# Voltage transfer characteristic of the CMOS inverter



 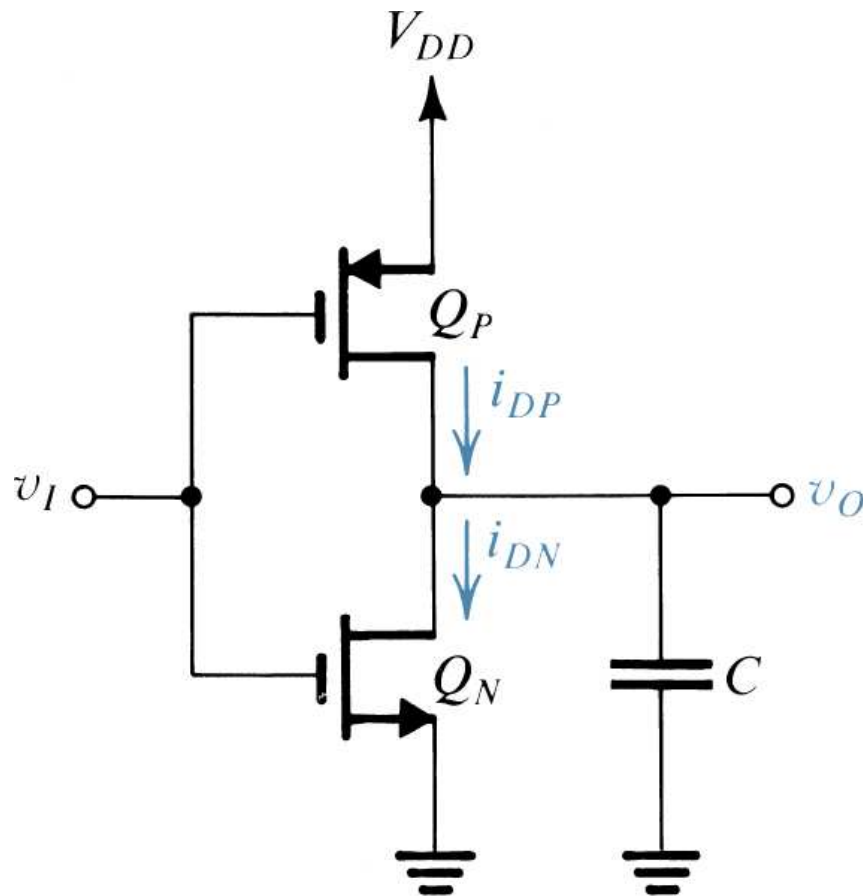
# Dynamic operation of a capacitive loaded CMOS inverter



equivalent circuit during the capacitor discharge.

 
# Dynamic operation of a capacitive loaded CMOS inverter




input and output waveforms

trajectory of the operating point as the input goes high and C discharges through the  $Q_N$


# Inverter layout

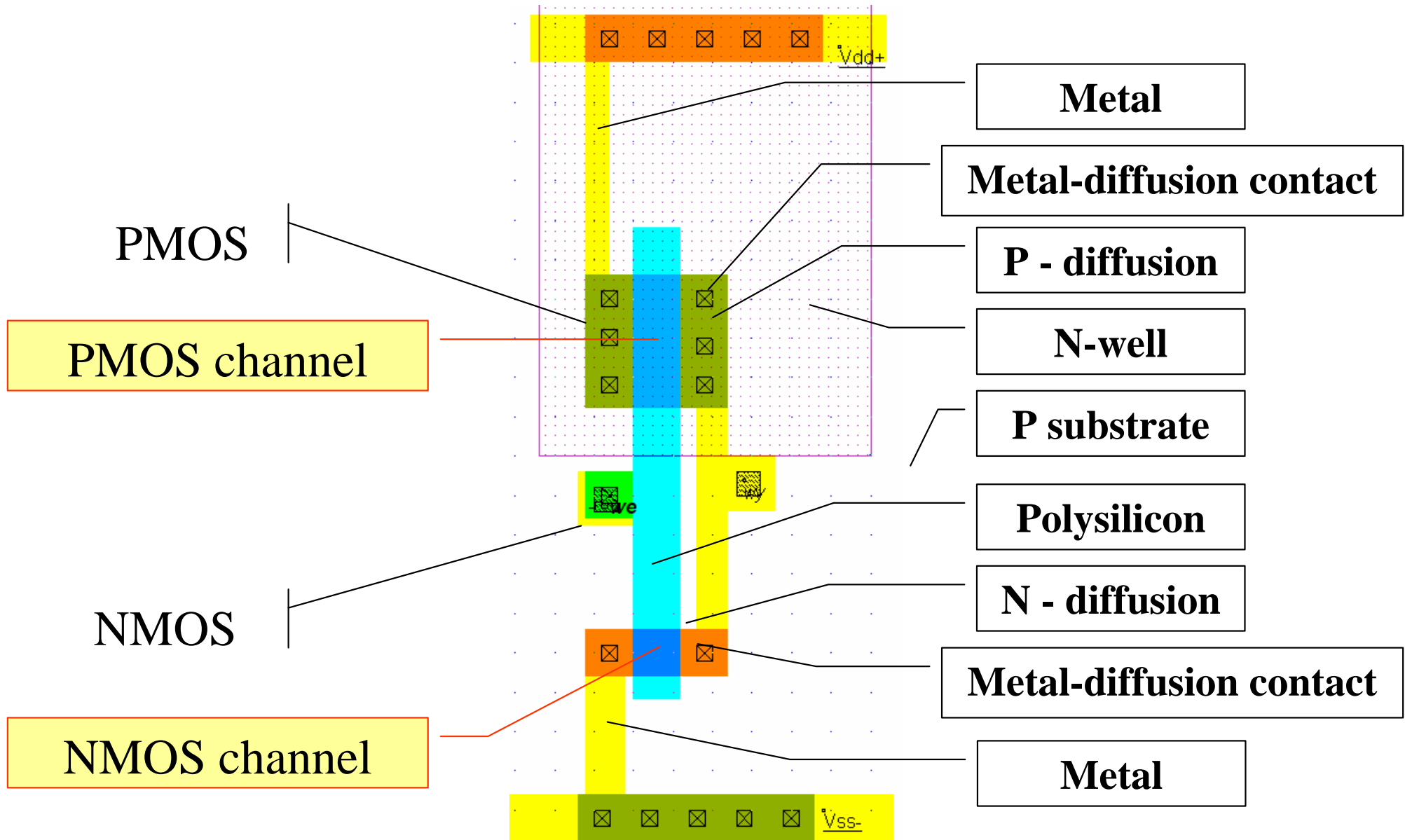


# NAND

 

# CMOS NAND gate

 


A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

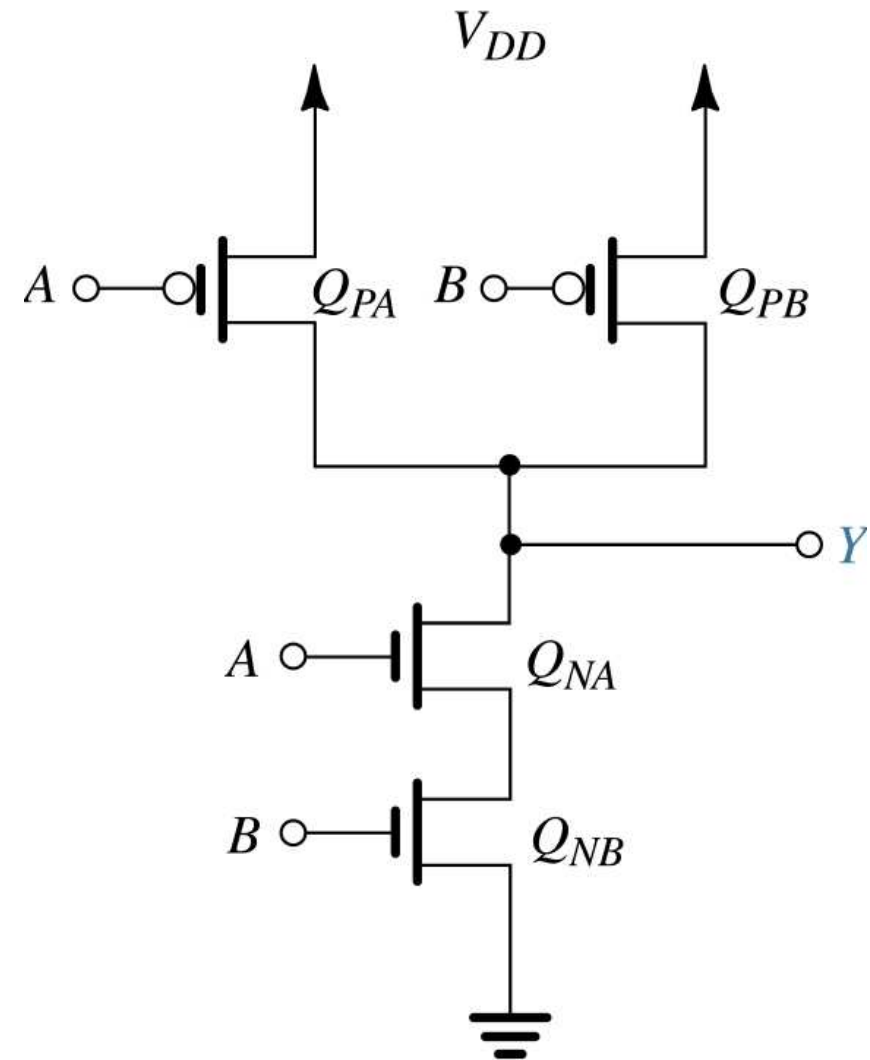

$$Y = \overline{AB}$$

# Gate size adjustment for NAND

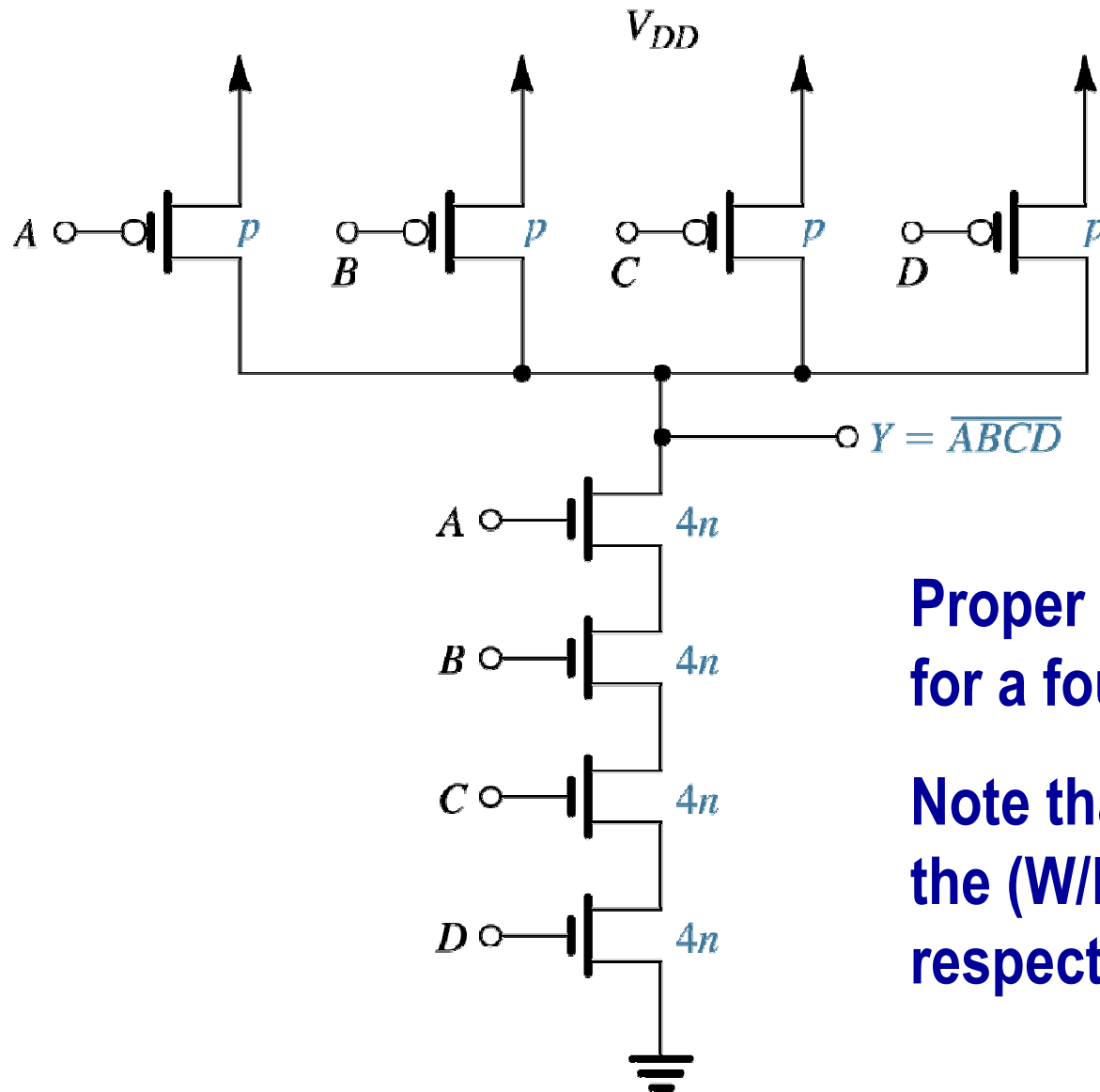


Proper transistor sizing  
for a four-input NAND gate.


Note that  $n$  and  $p$  denote  
the  $(W/L)$  ratios of  $Q_N$  and  $Q_P$ ,  
respectively, of the basic inverter.




# NAND layout

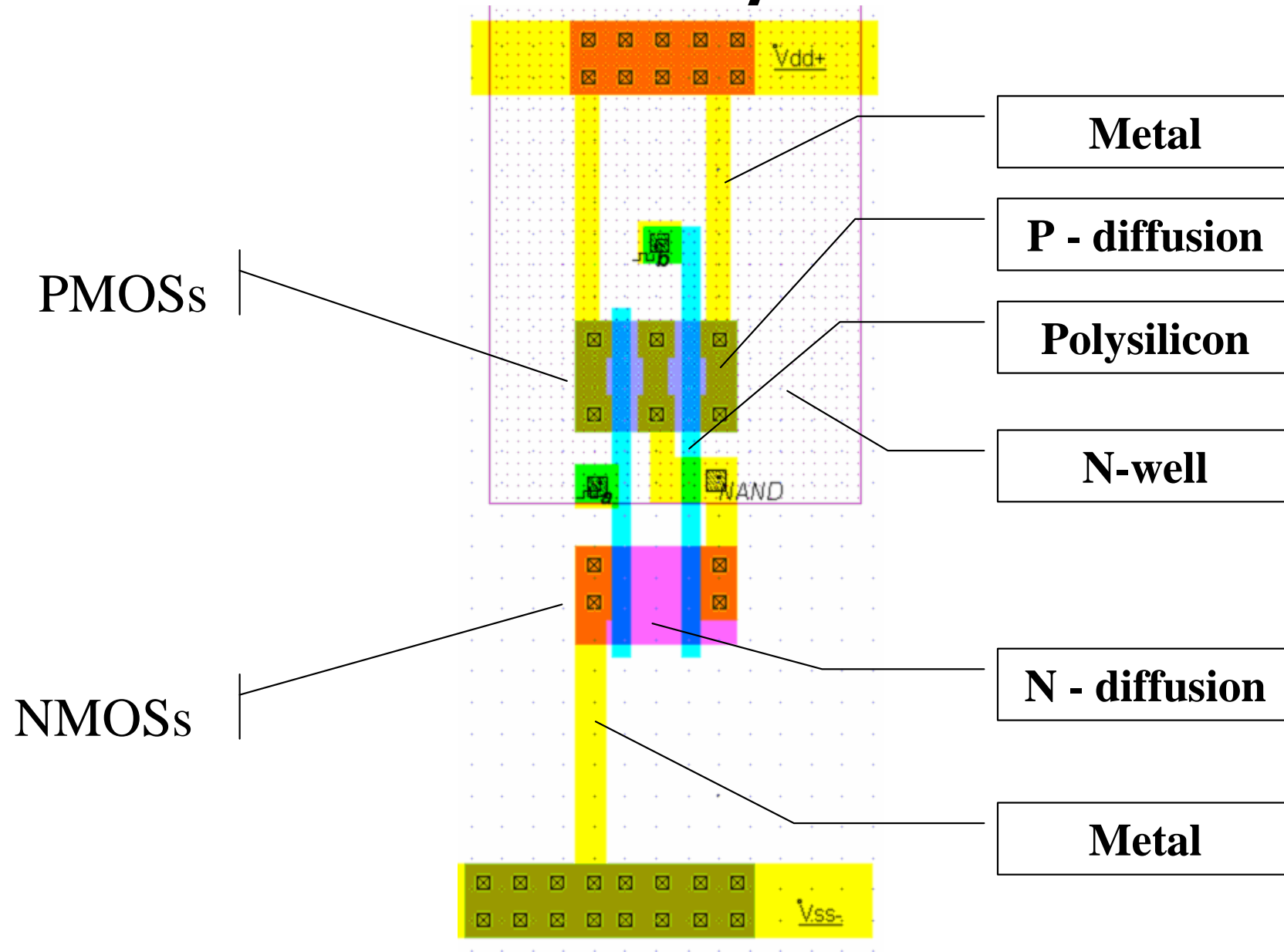


# NOR

 

# CMOS NOR gate

 


A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

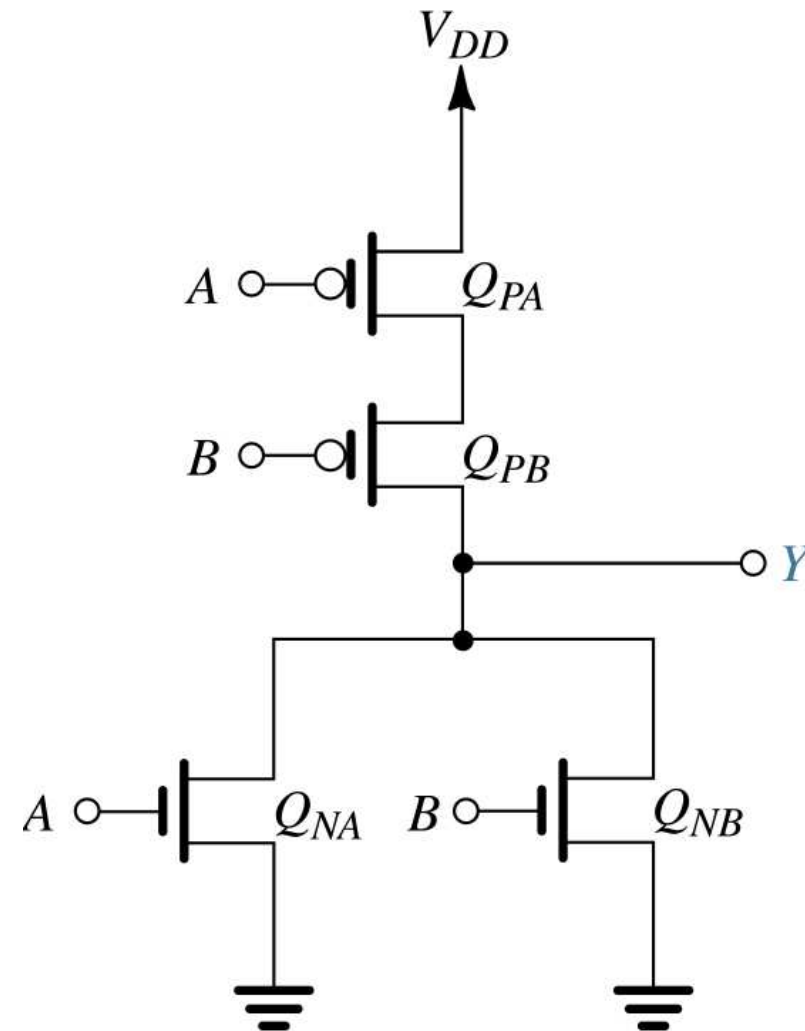

$$Y = \overline{A + B}$$


# Gate size adjustment for NOR

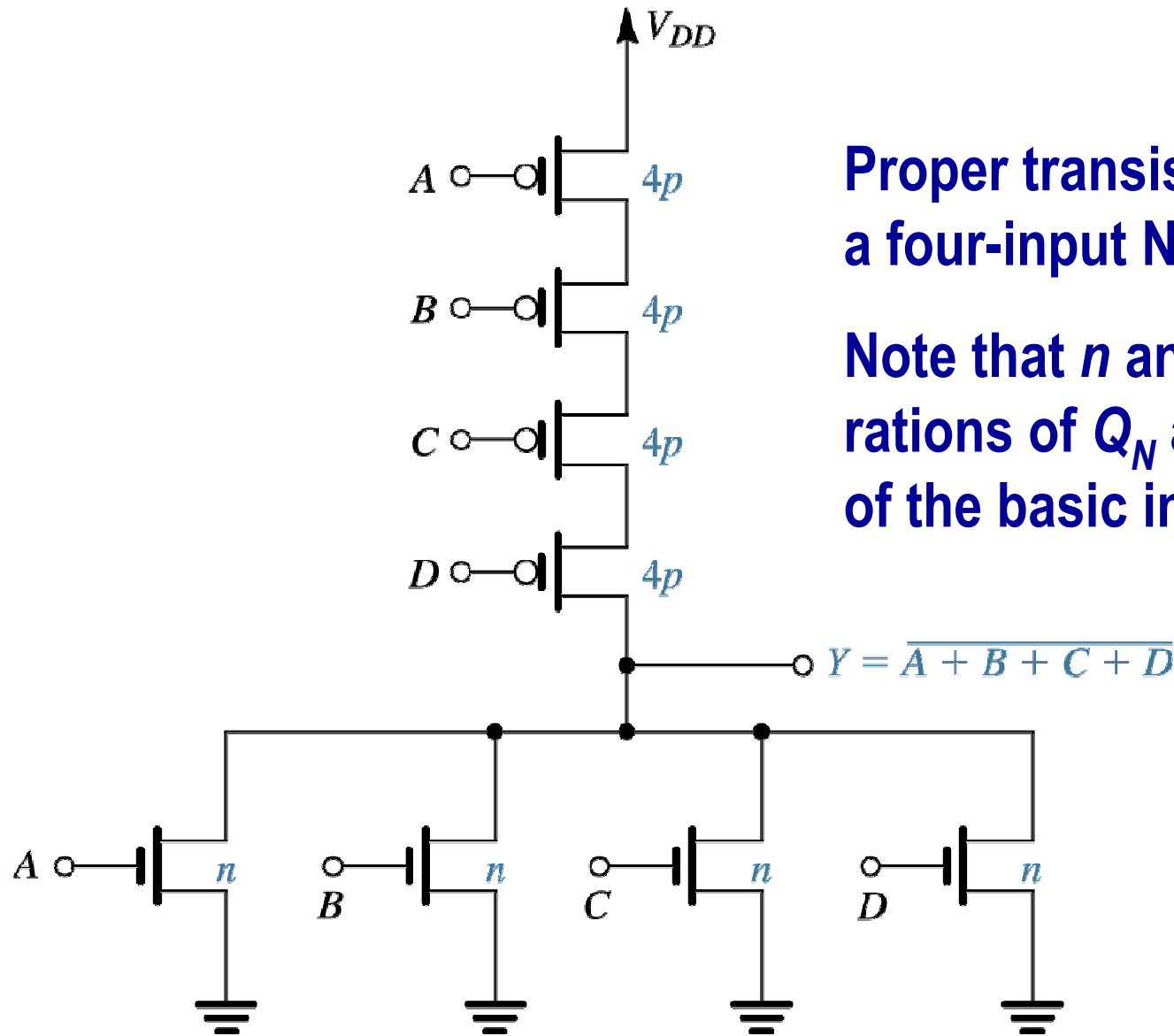


Proper transistor sizing for a four-input NOR gate.

Note that  $n$  and  $p$  denote the  $(W/L)$  ratios of  $Q_N$  and  $Q_P$ , respectively, of the basic inverter.


# NOR layout

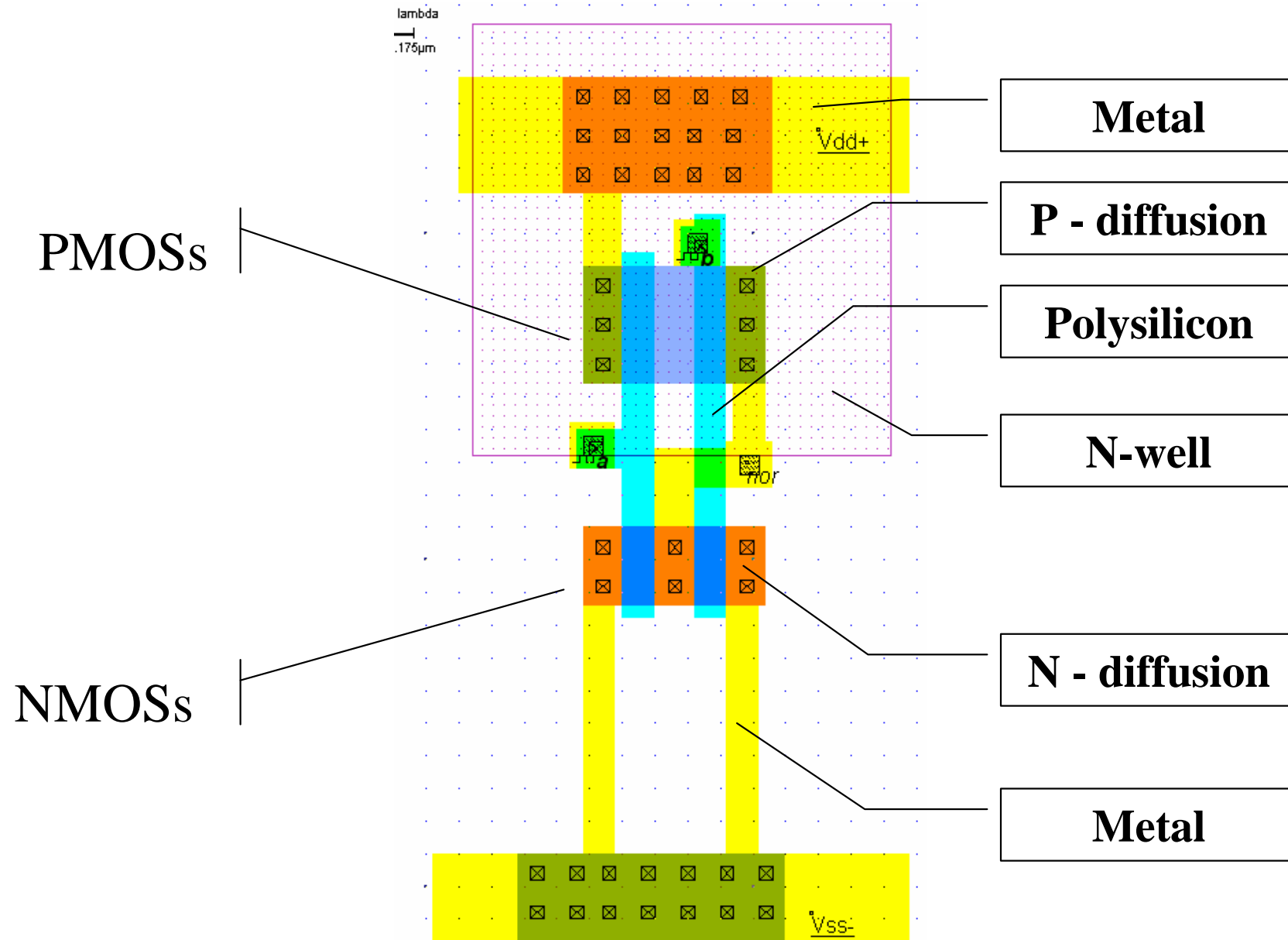


# Transmission gate

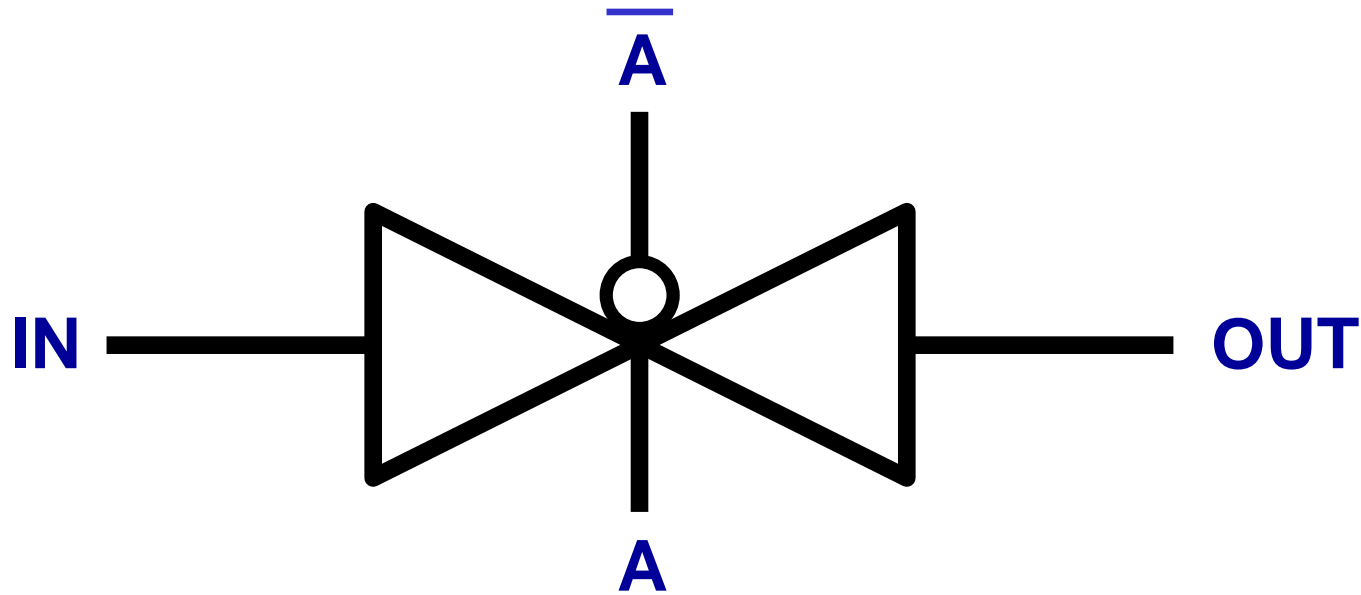

# Transmission gate


 


IN	A	OUT
0	0	H
0	1	0
1	0	H
1	1	1

 


$R_{on} = 100\Omega$  and  $R_{off} > 5 \text{ M}\Omega$  (high impedance H)

# Transmission gate layout

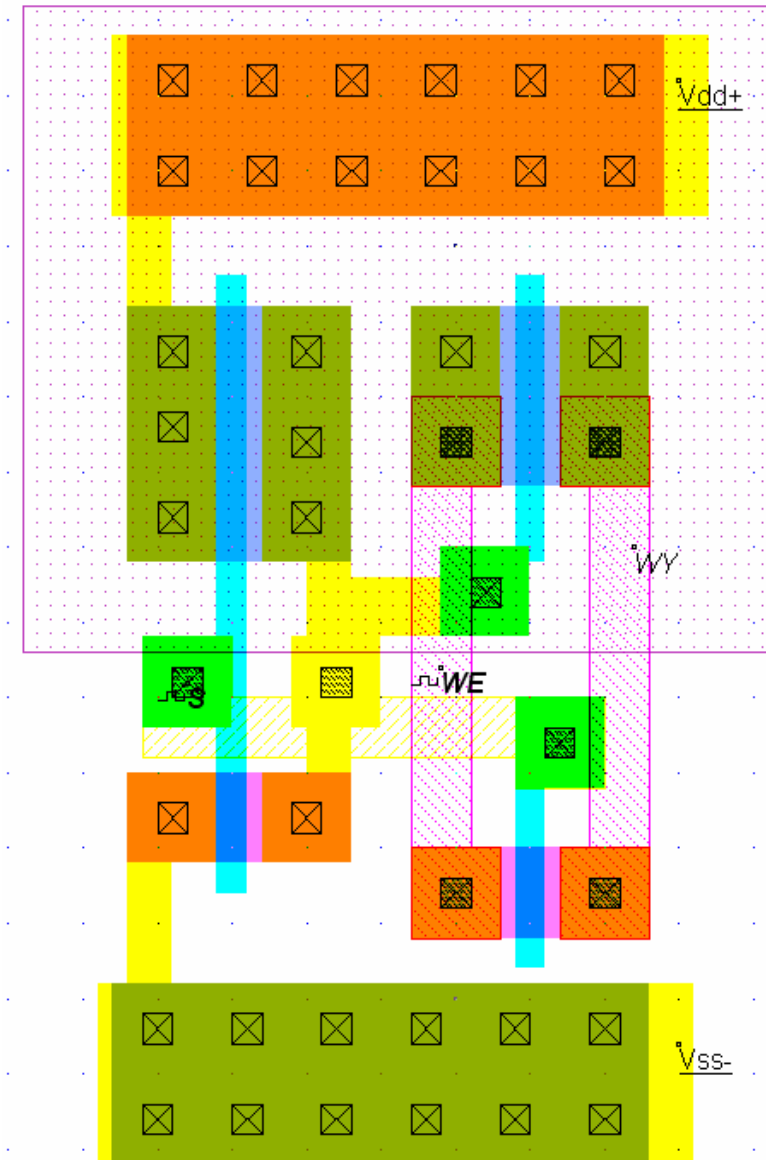
 





# XOR

 


# CMOS XOR

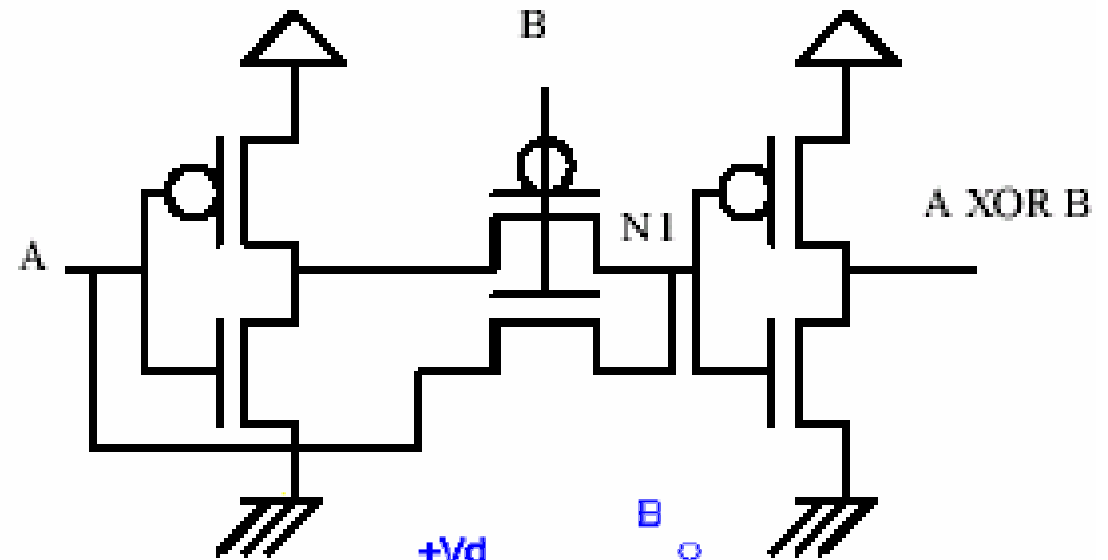 


A	B	A xor B
0	0	0
0	1	1
1	0	1
1	1	0

 

# XOR layout

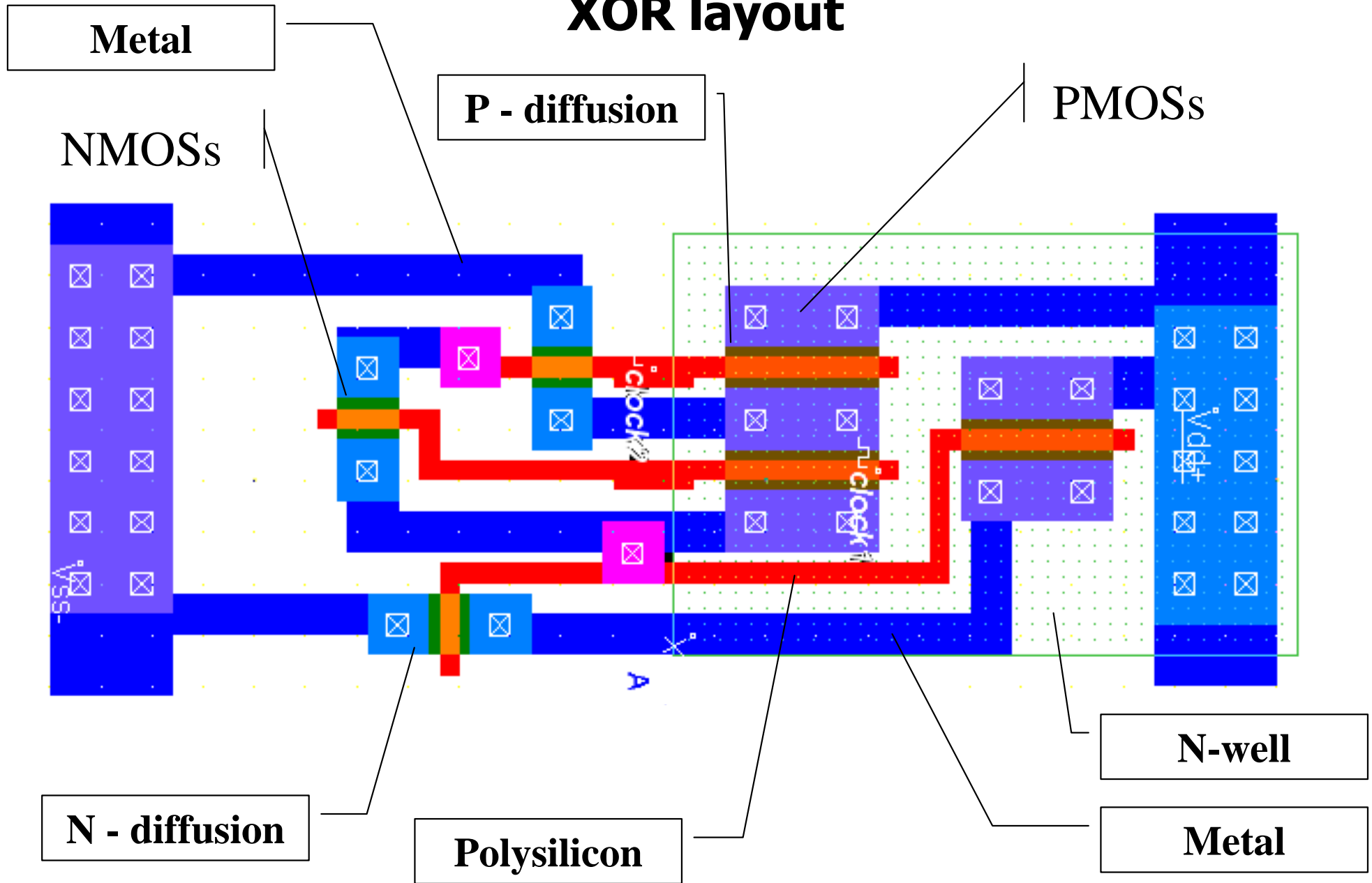


# Ring oscillator

 

**Formed by connecting three inverters in cascade**  
(Normally at least five inverters are used)


# Ring oscillator

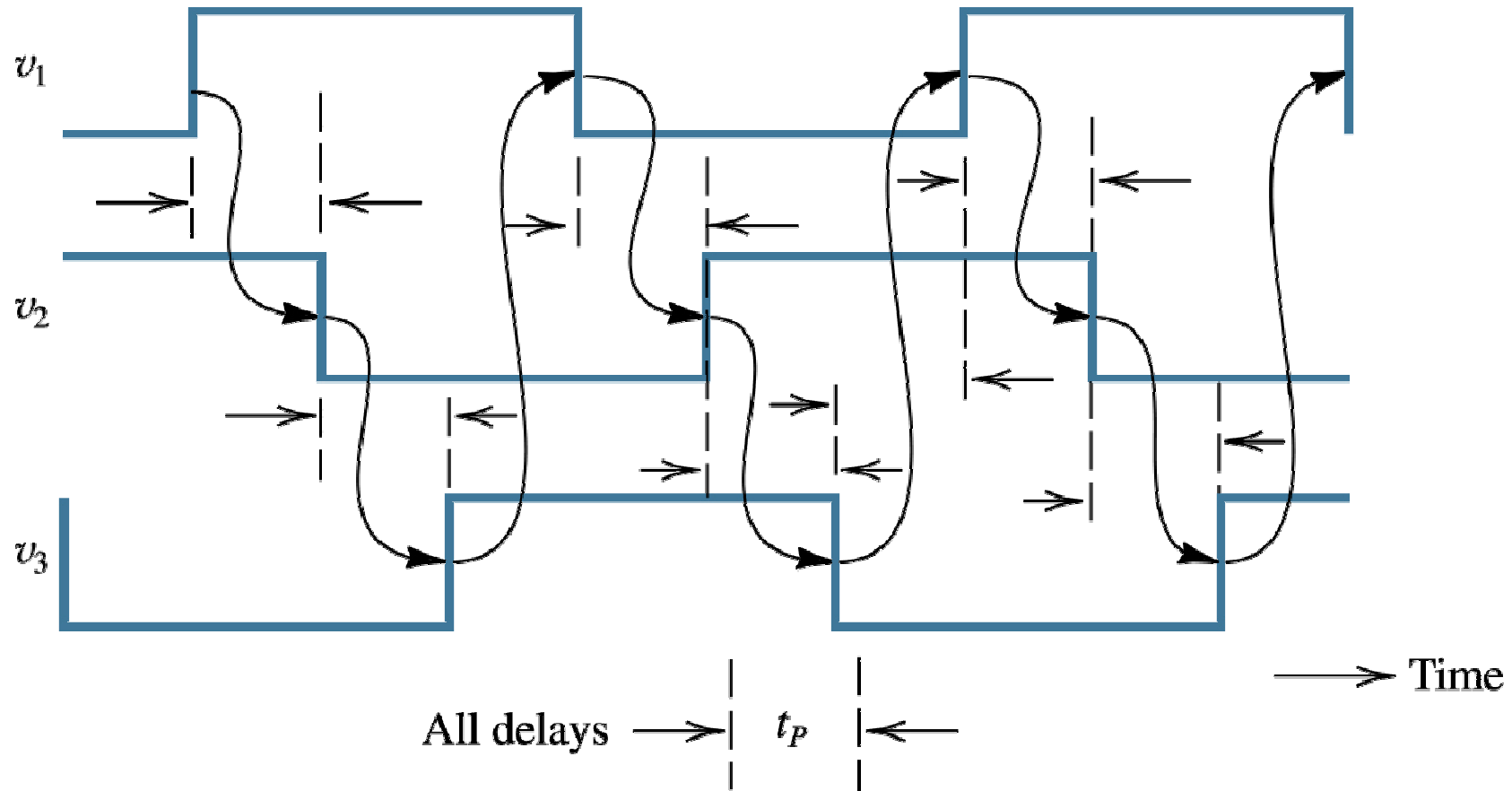


## The resulting waveform.

Observe that the circuit oscillates with frequency  $1/(6t_p)$ .

# Waveforms of ring oscillator

 

# Ring Oscillator (3 and 5 NOTs)

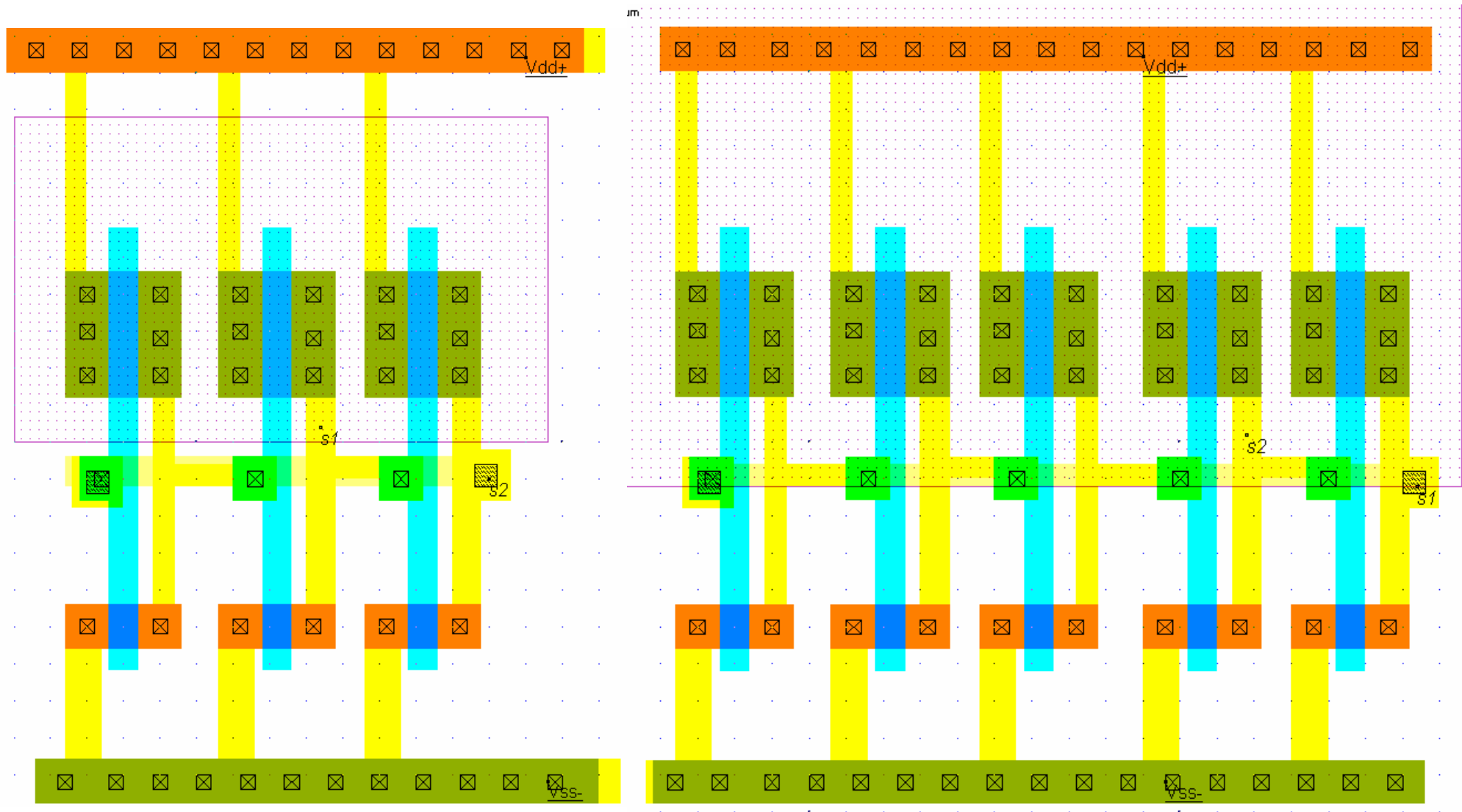

**Next lecture**

**More complex devices : MUX, flip-flops**

**Thank you for your attention**

