

Electronic Technology Design and Workshop IFE, B&T, V semester

Electronic Technology Design and Workshop

Presented and updated by
Przemek Sekalski
DMCS room 2

2007

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester

Electronic Technology Design and Workshop

Lecture 2

Electronic circuit analysis

Behind the stage by the example of MicroSim Spice

Technical University of Lodz
Department of Microelectronics and Computer Sciences


Electronic Technology Design and Workshop IFE, B&T, V semester 3

ETDW course road map

- ✓ Schematic edition, libraries of elements
- ✓ Circuit simulation & netlist generation
- ✓ Microelectronics - full custom design and simulation
- ✓ Microelectronics - simple layout synthesis
- ✓ Hardware description languages - behavioural description
- ✓ Logic & sequential synthesis - programmable logic devices
- ✓ PCB design – auto-routing

Project - bringing the pieces together

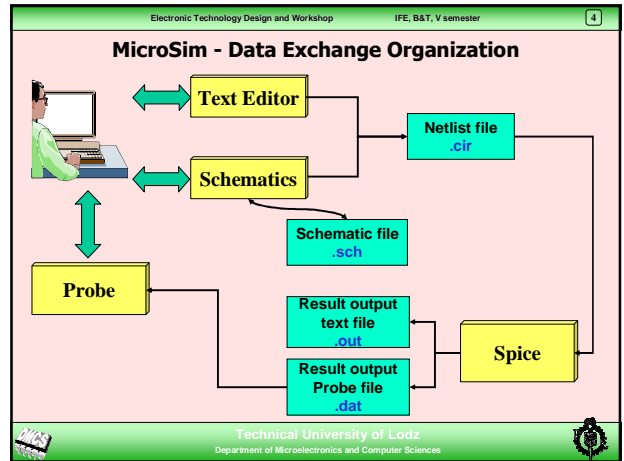Technical University of Lodz
Department of Microelectronics and Computer Sciences



Electronic Technology Design and Workshop IFE, B&T, V semester 5

How to move the project from the head to PC ?

Our "innovative" circuit

Let's try to put our idea into the MicroSim

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 6

How to move the project from the head to PC ?

How to convert ?
Which tool I need to use ?
What is available ?

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 7

MicroSim Text Editor

The **netlist** describes the connectivity of an electronic design.

To create the netlist there is need to define the **nodes**. Between the nodes the elements/parts are located.

Each time a part is used in a netlist, this is called an **instance**. Thus, each instance has a definition.

These definitions usually list the connections that can be made to that kind of device, and some basic properties of that device, i.e. **model**, **parameter's values**, etc.

These connection points are called **ports** or **pins**, among several other names.

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 8

MicroSim Text Editor – the nodes

There are three nodes and three elements

The ground node is called zero node by default

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 9

MicroSim Text Editor – the elements

Resistor **R**

Capacitor **C**

Solenoid, Coil **L**

MOS Transistors **M**

Diode **D**

Voltage source **V**

Current source **I**

... and many others

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 10

MicroSim Text Editor – the instances

Three elements corresponds to three instances

```
* Schematics Netlist *
R 1 2 1k
C 0 2 1n
V 1 0 DC 1
```

Asterisk are used to put the comment line

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 11

MicroSim Text Editor – the instances and libraries

- What does it mean the C, R and V for MicroSim ?
- What does it mean the DC ?
- Are there any other shortcuts, abbreviation symbols ?
- How and why the MicroSim understands the lines ?

The answer is ...

MODEL's LIBRARIES

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 12

MicroSim Text Editor – the libraries and models

- From electrical point of view each element might be described by the current **I** which goes through the element and voltage **U** measured over it.

The current-voltage characteristic of the resistor

Variables and constraints

$$U = R * I$$

Element parameter

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 13

MicroSim Text Editor – the instance

Name of the model

The element parameter list

The element name
Must be different for each element (letters and numbers are allowed, no space!)

The element nodes
indicate which current and voltage need to be used for calculation

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 14

MicroSim Text Editor – the Voltage Source instance

The voltage source might be DC (direct current) or AC (alternating current). Moreover the voltage might change in time.

DC – constant voltage amplitude in time, frequency is zero
VInput 1 0 DC 10

AC – constant voltage frequency in time,
VSource 1 0 AC 1 SIN(0V 0.2V 10kHz)

PULSE – defined trapezoid voltage pulse
V203 1 0 PULSE(-1mV 1mV 2ns 2ns 50ns 100ns)

Model_name/element_name nodes parameters

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 15

MicroSim Text Editor – the NMOS transistor instance

```

.MODEL N NMOS(LEVEL = 3
+ TOX = 1.8E-8 NSUB = 1.268366E16
+ GAMMA = 0.3246848 VTO = 0.6378109
+ DELTA = -0.6127926 UO = 532.5567276
+ ETA = 0.0688848 THETA = 0.0806494
+ VMAX = 1.923644E5 KAPPA = 4.192879E-3 RSH = 654.5658635
+ IS = 1.126041E-14 NFS = 3.598738E11 XJ = 1E-9
+ WD = 4.21328E-7 CGDO = 2.907231E-10 CGSO = 2.907231E-10
+ CGBO = 3.586291E-9 CJ = 2.37583E-4 PB = 0.6279748
+ MJ = 0.381556 FC = 0.5 CJSW = 7.38563E-10
+ MJSW = 0.148419 LD = 8.861389E-9)
  
```

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 16

MicroSim Text Editor – the libraries

The libraries are the set of models i.e. analogue basic components, diodes, transistors, etc

There are possibility to write down your own model and build your own libraries

To include the given library into to project there is need to type the command **.INCLUDE {name of the library}**

To write your model using the predefined one type **.MODEL {name} {type}**

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 17

MicroSim – the simulation

How to get the results ?

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 18

MicroSim - Data Exchange Organization

```

* Sample RC circuit netlist
R 1 2 1k
C 0 2 1n
U 1 0 DC 1
.END
  
```

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 19

SPICE - general information

Simulation Program with Integrated Circuit Emphasis is a general purpose analogue circuit simulator.

It is a powerful program that is used in integrated circuit (IC) and board-level design to check the integrity of circuit designs and to predict circuit behaviour.

The input data are written in **.cir** files as the netlist.

The details about SPICE will be given in the next lecture.

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 20

MicroSim - Data Exchange Organization

* Sample RC circuit netlist
R 1 2 1k
C 0 2 1n
U 1 0 DC 1
.END

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 21

SPICE - .out file

```
**** 09/29/107 13:30:13 ***** NT PSpice 8.0 (July 1997) ***** ID# 87788 ****
* RC
**** CIRCUIT DESCRIPTION
*****
R 1 2 1k
C 2 0 1n
V 1 0 DC 1
**** 09/29/107 13:30:13 ***** NT PSpice 8.0 (July 1997) ***** ID# 87788 ****
* RC
**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C
*****
NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE
( 1) 1.0000 ( 2) 1.0000
VOLTAGE SOURCE CURRENTS
NAME CURRENT
V 0.000E+00
TOTAL POWER DISSIPATION 0.00E+00 WATTS
JOB CONCLUDED
TOTAL JOB TIME .05
```

Date and general information about the SPICE version

Circuit description netlist

Simulation constraints

Simulation results Voltage in all nodes

General infos about simulation, i.e. power dissipation, simulation time

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 22

The answer is ...

For $U = 1V$ the $U_c = 1V$!!!
Because $U_c = V(2) - V(0) = 1 - 0 = 1V$
No current flow through capacitor ;)

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 23

DC analysis

The input voltage varies from -5V to +5V with step 0.1V.

There is need to perform 100 times the same calculation with different settings for voltage source **V**.

It might be easily done by SPICE just by using the directives **.DC** which is responsible for DC analysis.

```
.DC {name of the source} {min} {max} {step}
.DC V -5 5 .1
.PROBE
```

Probe is a tool for simulation results visualisation

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 24

PROBE DC Analysis

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 25

AC Analysis

The frequency of input voltage varies from 1 Hz to 100 MHz.

With constant step i.e. 10 Hz there is 10 millions step !!!

Lets make 10 steps for each decade
(10 20 30 ...100 200 300... 1k 2k 3k... 10k 20k 30k... 100k 100Meg)

The SPICE directive is **.AC**

```
.V 1 0 DC 1 AC 1
.AC [LIN][OCT][DEC] {points} {start freq} {end freq}
.AC OCT 10 1 100Meg
.PROBE
```

And check the results once again

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 26

PROBE AC analysis

voltage

High pass filter

frequency

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 27

Transient Analysis

We would like to know what will happen when the voltage will arise from 0 to 1 V and back to 0 V.

We need to perform a transient analysis (non-stationary conditions)

The SPICE directive is **.TRAN**

```
.V 1 0 DC 1 AC 1 PULSE 0 1 1u 0.001u 0.001u 10u 20u
.TRAN {print step value} {final time}
.TRAN 0.001u 20u
.PROBE
```

And check the results once again

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 28

Transient analysis

voltage

In red is a input pulse V
PULSE 0 1 1u 0.001u 0.001u 10u 20u
PULSE((v1) (v2) {tdelay} {trise}
+ {tfall} {width} {period})
In green is a U_c

time

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 29

Other Analyses

- Temperature Analysis **.TEMP**
.TEMP {value}* Examples: .TEMP 0 27 125
- Sensitivity Analysis **.SENS**
.SENS {output variable}* Examples: .SENS V(9) V(4,3) I(VCC)
- Noise Analysis **.NOISE**
.NOISE {output variable} {name} [{print interval}]
Examples: .NOISE V(5) VIN
- Fourier Analysis **.FOUR**
.FOUR {freq} {output var}*
Examples: .FOUR 10KHz v(5) v(6,7)



Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 30

The Spice Units

F	E-15	femto
P	E-12	pico
N	E-9	nano
U	E-6	micro
M	E-3	milli
K	E+3	kilo
MEG	E+6	mega
G	E+9	giga
T	E+12	tera

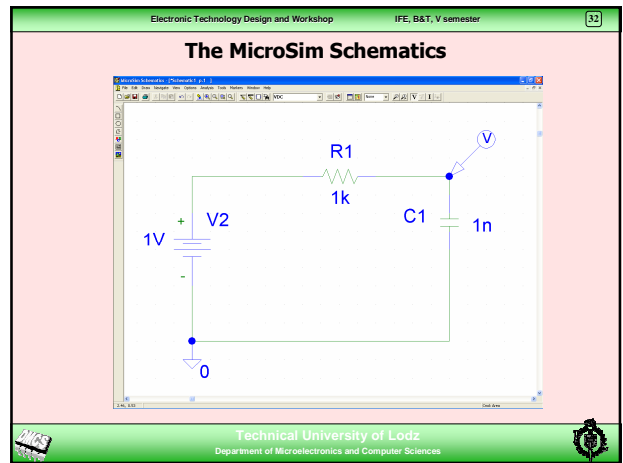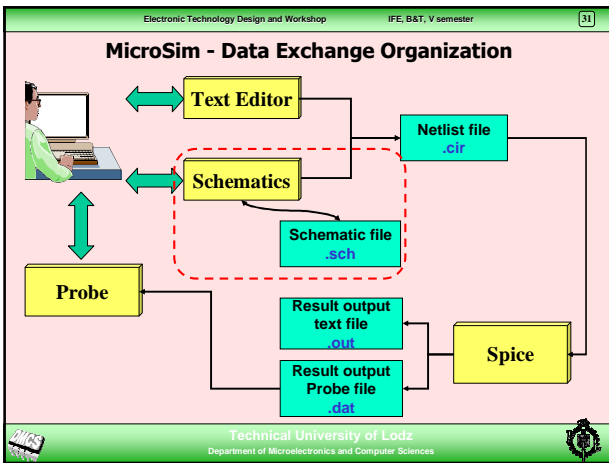Technical University of Lodz
Department of Microelectronics and Computer Sciences



Electronic Technology Design and Workshop IFE, B&T, V semester 33

The MicroSim Schematics - life is easy

One click


*** Schematics Netlist ***

```

R_R1    $N_0002 $N_0001 1k
C_C1    0 $N_0001 1n
V_V2    $N_0002 0 1V
          
```

The netlist is generated automatically
The simulation settings are accessible via GUI

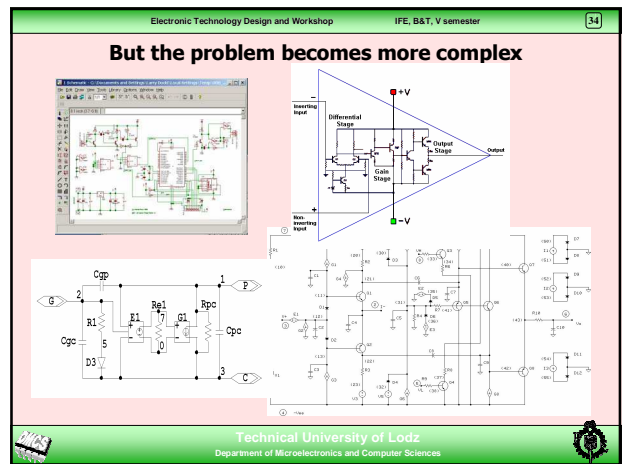Technical University of Lodz
Department of Microelectronics and Computer Sciences



Electronic Technology Design and Workshop IFE, B&T, V semester 35

The SPICE is also available through WWW

<http://spice.dmcs.p.lodz.pl/>

Technical University of Lodz
Department of Microelectronics and Computer Sciences

Electronic Technology Design and Workshop IFE, B&T, V semester 36

The next lecture

The SPICE – behind the GUI

Thank you for your attention

Technical University of Lodz
Department of Microelectronics and Computer Sciences

