

Electronic Technology Design and Workshop

Presented and updated by
Przemek Sekalski
DMCS room 2

2007



Electronic Technology Design and Workshop

Lecture 3 Electronic circuit analysis The SPICE – behind the GUI




ETDW course road map

- ✓ Schematic edition, libraries of elements
- ✓ **Circuit simulation & netlist generation**
- ✓ Microelectronics - full custom design and simulation
- ✓ Microelectronics - simple layout synthesis
- ✓ Hardware description languages - behavioural description
- ✓ Logic & sequential synthesis - programmable logic devices
- ✓ PCB design – auto-routing


📁 Project - bringing the pieces together




MicroSim - Data Exchange Organization

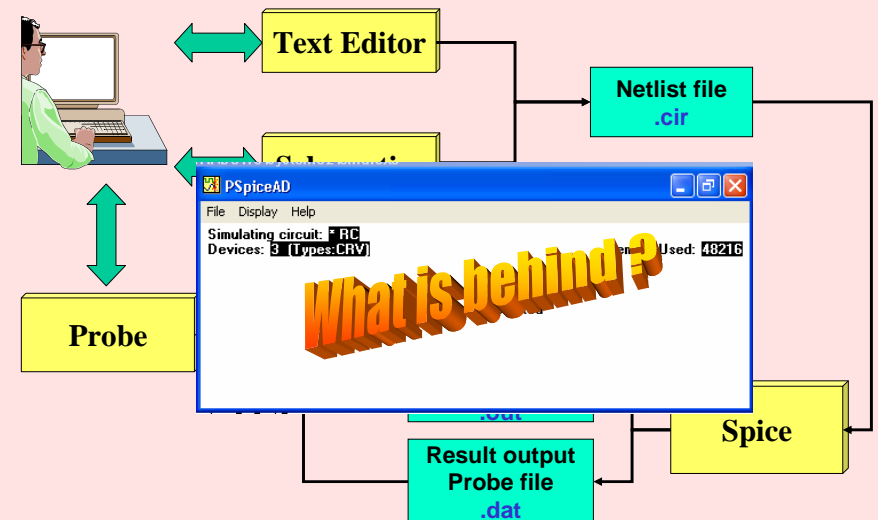

Circuit scheme

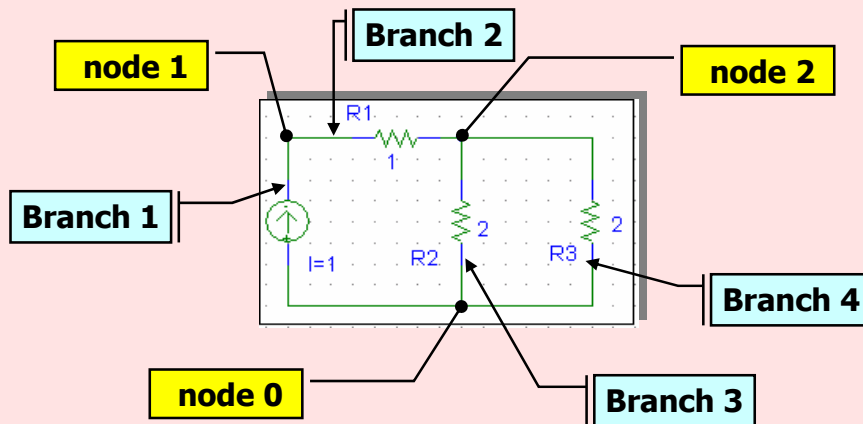

Fundamental branch


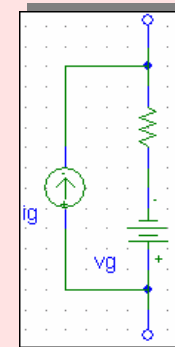


Fundamental branch consist of:

- Voltage source
- Current source
- Impedance




Network Graph – circuit topology

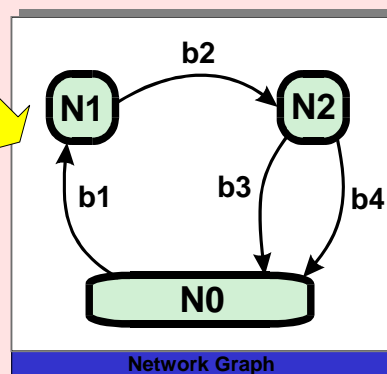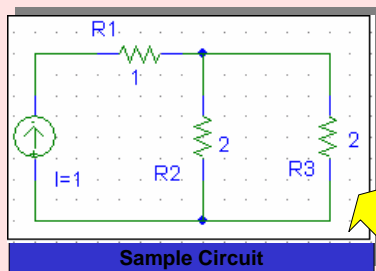

Notice that all branches are **oriented** !



Circuit topology

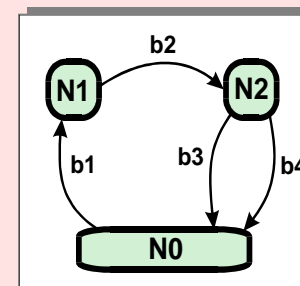

- Nodes: N_0, N_1, N_2
- Branches: b_1, b_2, b_3, b_4
- Nodal voltages: V_{N_1}, V_{N_2}
- Branch Voltages: $V_{b_1}, V_{b_2}, V_{b_3}, V_{b_4}$
- Branch Currents $I_{b_1}, I_{b_2}, I_{b_3}, I_{b_4}$



Vector representation

$$\mathbf{V}_b = \begin{bmatrix} V_{b1} \\ V_{b2} \\ \vdots \\ V_{bM} \end{bmatrix} \quad \mathbf{I}_b = \begin{bmatrix} I_{b1} \\ I_{b2} \\ \vdots \\ I_{bM} \end{bmatrix} \quad \mathbf{V}_n = \begin{bmatrix} V_{n1} \\ V_{n2} \\ \vdots \\ V_{nN} \end{bmatrix} = ?$$

Branch Voltages
Branch Currents
Nodal Voltages


We are looking for nodal voltages ?



Kirchhoff's Current Law

For each node

$$\sum_{i=1}^z I_i = 0$$

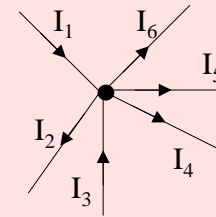

For one sample node we can write

$$I_1 - I_2 + I_3 - I_4 - I_5 - I_6 = 0$$

How to generalize for all nodes?



Incidence matrix



To apply **Kirchhoff's Current Law** to whole circuit,
let's create the term:

INCIDENCE MATRIX - A

$$a_{kj} = \begin{cases} 1 & \text{if current } i_j \text{ leaves node } k \\ -1 & \text{if current } i_j \text{ enters node } k \\ 0 & \text{if } i_j \text{ neither enters nor leaves node } k \end{cases}$$



Extraction from .CIR file

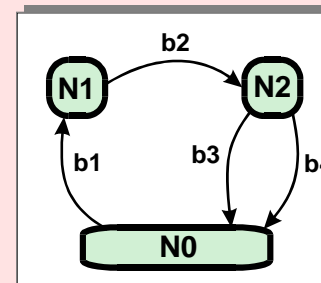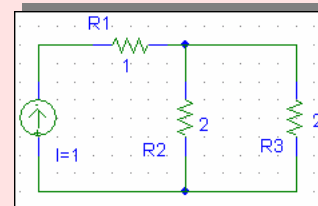

Circuit Netlist

* Sample circuit

```
I1 1 0 1
R1 1 2 1
R2 2 0 2
R3 2 0 2
```

```
.DC
.END
```



Incidence matrix generating


```

Circuit Netlist
* Sample circuit
I1 1 0 1
R1 1 2 1
R2 2 0 2
R3 2 0 2

.DC
.END

```
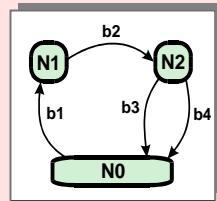
$$\mathbf{A} = \begin{bmatrix} 1 & 0 & -1 & -1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{matrix} N0 \\ N1 \\ N2 \end{matrix}$$



Incidence matrix vs reduced incidence matrix

$$\mathbf{A} = \begin{bmatrix} 1 & 0 & -1 & -1 \\ -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix}$$

Can we remove one row without losing the information ?

$$\mathbf{A}_{reduced} = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix}$$



Kirchhoff's Current Law


$$\mathbf{A} \mathbf{I}_b = 0$$

Matrix representation

$$\mathbf{A}_r \mathbf{I} = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_{I1} \\ I_{R1} \\ I_{R2} \\ I_{R3} \end{bmatrix} = 0$$

Equation set representation
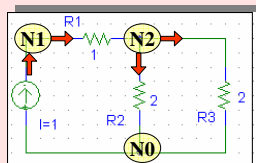
$$\begin{cases} -I_{I1} + I_{R1} = 0 \\ -I_{R1} + I_{R2} + I_{R3} = 0 \end{cases}$$



The Ohm's law

To get relationship between branch voltages v_b and branch currents i_b , let's use Ohm's Law:

$$\mathbf{v}_b = \mathbf{r}_b \mathbf{i}_b$$

or

$$\mathbf{i}_b = \mathbf{y}_b \mathbf{v}_b$$

For the whole circuit we need to move to matrix representation


$$\mathbf{V}_b = \mathbf{R}_b \mathbf{I}_b \quad \mathbf{I}_b = \mathbf{Y}_b \mathbf{V}_b$$

\mathbf{R}_b – branch resistance (impedance) matrix

\mathbf{Y}_b – branch admittance matrix



Admittance matrix and sources vector

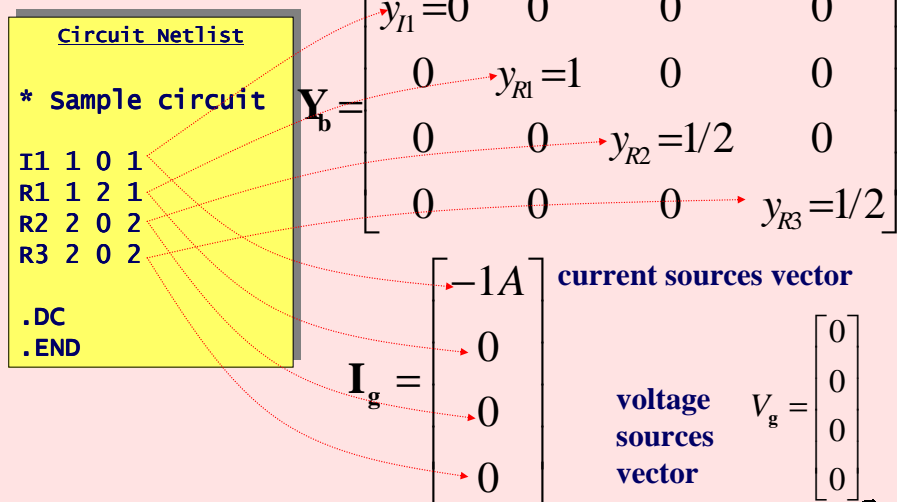

Branch current with independent current source

But independent current and voltage sources also must be considered, so:

$$I_b = I_b^* - (I_g - Y_b V_g)$$

and because there's no voltage on current sources, we have:

$$I_b^* = Y_b V_b$$

and finally:

$$I_b = Y_b V_b - (I_g - Y_b V_g)$$



Some maths

$$A I_b = 0$$

$$I_b = Y_b V_b - I_g + Y_b V_g$$

$$A (Y_b V_b - I_g + Y_b V_g) = 0$$

$$A Y_b V_b - A I_g + A Y_b V_g = 0$$

$$A Y_b V_b = A (I_g - Y_b V_g)$$

... but the number of branches might be huge in comparison to number of nodes ...



Nodal voltage vs branch voltage

If there's taken to consideration that number of nodes is always less or equal than number of branches it is convenient to use Nodal-Voltage Vector V_n in place of Branch-Voltage Vector V_b

Relation between V_n and V_b is following:

$$V_b = A^T V_n$$

so finally we get



Fundamental relation for all linear networks

$$\mathbf{V}_b = \mathbf{A}^T \mathbf{V}_n$$

$$\mathbf{A} \mathbf{Y}_b \mathbf{V}_b = \mathbf{A} (\mathbf{I}_g - \mathbf{Y}_b \mathbf{V}_g)$$

$$\mathbf{A} \mathbf{Y}_b \mathbf{A}^T \mathbf{V}_n = \mathbf{A} (\mathbf{I}_g - \mathbf{Y}_b \mathbf{V}_g)$$

what might be rewritten to

$$\mathbf{Y}_n \mathbf{V}_n = \mathbf{I}_n$$

where

\mathbf{Y}_n - Node-Admittance Matrix

\mathbf{I}_n - Node-Current Matrix



Solutions and solvers


To solve **system of linear equations** we need to use one of the common methods as

- Elimination of variables
- Row reduction (Gauss elimination)
- Cramer's rule
- LU decomposition
- other methods




Example


Let's identify the branches and nodes

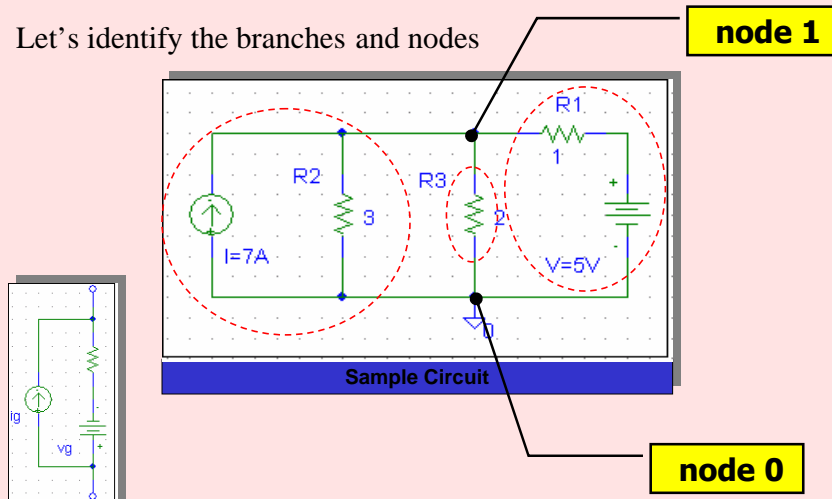

Example

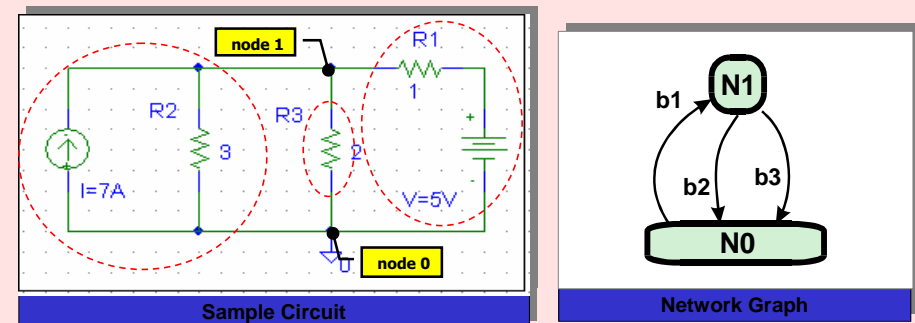

Matrices generation

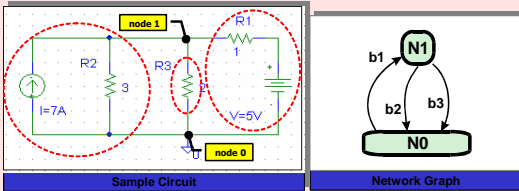

$$\mathbf{A} = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix}$$

$$\mathbf{Y}_b = \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \quad \mathbf{I}_g = \begin{bmatrix} 0 \\ 0 \\ 7 \end{bmatrix} \quad \mathbf{V}_g = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$



Putting the numbers into equation

$$\mathbf{A} = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \quad \mathbf{Y}_b = \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \quad \mathbf{I}_g = \begin{bmatrix} 0 \\ 0 \\ 7 \end{bmatrix} \quad \mathbf{V}_g = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\mathbf{A} \mathbf{Y}_b \mathbf{A}^T \mathbf{V}_n = \mathbf{A} (\mathbf{I}_g - \mathbf{Y}_b \mathbf{V}_g)$$

$$\begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} [\mathbf{V}_{n1}] = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \left(\begin{bmatrix} 0 \\ 0 \\ 7 \end{bmatrix} - \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \right)$$



$$\begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} [\mathbf{V}_{n1}] = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \left(\begin{bmatrix} 0 \\ 0 \\ 7 \end{bmatrix} - \begin{bmatrix} 1 & 0 & 0 \\ 0 & \frac{1}{2} & 0 \\ 0 & 0 & \frac{1}{3} \end{bmatrix} \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \right)$$

$$\begin{bmatrix} -1 & \frac{1}{2} & \frac{1}{3} \end{bmatrix} \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} [\mathbf{V}_{n1}] = \begin{bmatrix} -1 & 1 & 1 \end{bmatrix} \left(\begin{bmatrix} 0 \\ 0 \\ 7 \end{bmatrix} - \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \right)$$

$$\left(1 + \frac{1}{2} + \frac{1}{3}\right) [\mathbf{V}_{n1}] = 5 + 7$$

$$\frac{11}{6} \mathbf{V}_{n1} = 12$$

$$\mathbf{V}_{n1} = 6.545 \text{ volt}$$



Summary

- All electronics circuits might be represented by system of equations
- It is easy to extract the parameters from netlist (.cir file)
- The system of equation is solved using the common methods
- Knowledge about the all nodal voltages allows to find any necessary value (currents, power, etc)



Thank you for your attention

