


Design Entry

- ◆ Hierarchical schematic
- ◆ Finite state machine
- ◆ Hardware description language (HDL)
 - ◆ PALASM
 - ◆ Abel
 - ◆ AHDL
 - ◆ Verilog (IEEE 1364-2001)
 - ◆ VHDL (IEEE 1076-2001)
 - ◆ SystemC


VHDL - Behavioral Description

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```
 
```
entity andor is  
port(  
  A : in STD_LOGIC;  
  B : in STD_LOGIC;  
  C : in STD_LOGIC;  
  Y : out STD_LOGIC  
);  
end andor;
```


 
```
architecture behavioral of andor is  
begin  
  Y <= (A and B) or C;  
end behavioral;
```



VHDL - Structural Description

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```



```
entity andor is  
port(  
  A : in STD_LOGIC;  
  B : in STD_LOGIC;  
  C : in STD_LOGIC;  
  Y : out STD_LOGIC  
);  
end andor;
```

```
architecture structural of andor is  
  signal int : STD_LOGIC;
```

```
  component AND2  
  port ( i0 : in STD_LOGIC;  
         i1 : in STD_LOGIC;  
         O : out STD_LOGIC);  
  end component;
```

```
  component OR2  
  port ( i0 : in STD_LOGIC;  
         i1 : in STD_LOGIC;  
         O : out STD_LOGIC);  
  end component;
```
  
```
begin  
  U1 : AND2  
    PORT MAP (I0=>b, I1=>a, O=>int);  
  U2 : OR2  
    PORT MAP (I0=>c, I1=>int, O=>y);  
end structural;
```




Flip-Flop

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity flipflop is
    Port ( D : in std_logic;
          Q : out std_logic;
          C : in std_logic);
end flipflop;

 architecture behavioral of flipflop is
begin
    process (C)
    begin
        if C'event and C='1' then -- C rising edge
            Q <= D;
        end if;
    end process;
end behavioral;
```



Flip-Flop with Preset and Clear

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity flipflop is
```

```
    Port ( D : in std_logic;  
          R : in std_logic;  
          S : in std_logic;  
          Q : out std_logic;  
          C : in std_logic);
```

```
end flipflop;
```

```
architecture behavioral of flipflop is  
begin
```

```
    process (C,R,S)
```

```
    begin
```

```
        if R = '1' then
```

```
            Q <= '0';
```

```
        elsif S = '1' then
```

```
            Q <= '1';
```


```
        elsif C'event and C='1' then  -- C rising edge
```

```
            Q <= D;
```

```
        end if;
```

```
    end process;
```

```
end behavioral;
```

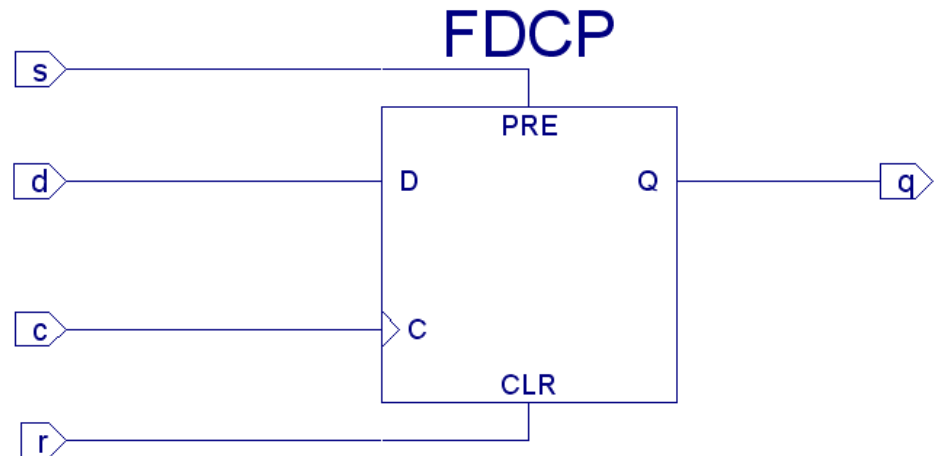


Flip-Flop with Set and Reset

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity flipflop is
    Port ( D : in std_logic;
          R : in std_logic;
          S : in std_logic;
          Q : out std_logic;
          C : in std_logic);
end flipflop;

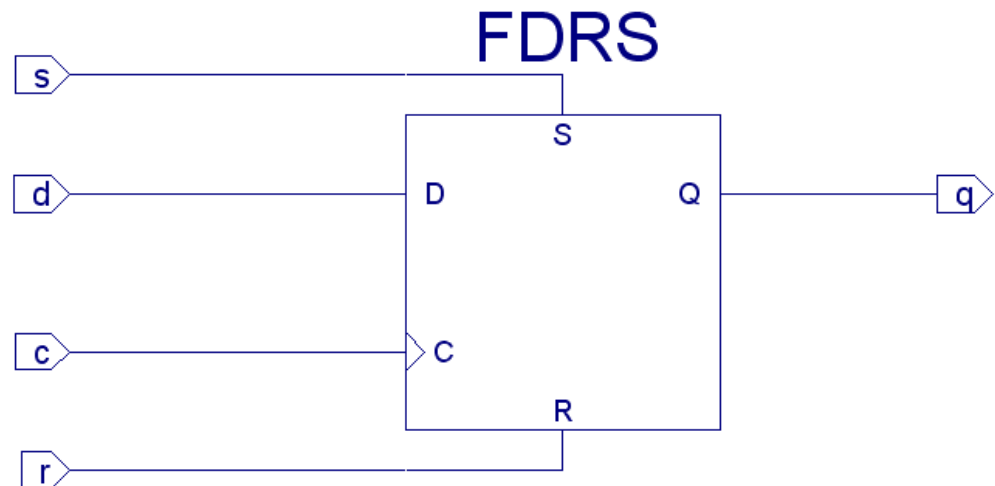architecture behavioral of flipflop is
begin
    process (C)
    begin
        if C'event and C='1' then -- C rising edge
            if R='1' then
                Q <= '0';
            elsif S='1' then
                Q <= '1';
            else
                Q <= D;
            end if;
        end if;
    end process;
end behavioral;
```



Video Signal Generator

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;

-- VGA Video Sync generation

ENTITY VGA_SYNC IS

PORT(clock_25Mhz, red, green, blue: IN  STD_LOGIC;
      red_out, green_out, blue_out,
      horiz_sync_out, vert_sync_out: OUT STD_LOGIC;
      pixel_row, pixel_column : OUT STD_LOGIC_VECTOR(9 DOWNTO 0));

END VGA_SYNC;
```



Video Signal Generator

ARCHITECTURE a OF VGA_SYNC IS

```
SIGNAL horiz_sync, vert_sync : STD_LOGIC;  
SIGNAL video_on, video_on_v, video_on_h : STD_LOGIC;  
SIGNAL h_count, v_count : STD_LOGIC_VECTOR(9 DOWNTO 0);
```

BEGIN

```
-- video_on is high only when RGB data is being displayed
```

```
video_on <= video_on_H AND video_on_V;  
horiz_sync_out    <= horiz_sync;  
vert_sync_out     <= vert_sync;  
pixel_column <= h_count;  
pixel_row <= v_count;
```


Video Signal Generator

```
-- Generate Horizontal and Vertical Timing Signals for Video Signal
```

```
PROCESS
```

```
BEGIN
```

```
WAIT UNTIL (clock_25Mhz'EVENT) AND (clock_25Mhz='1');
```

```
-- H_count counts pixels (640 + extra time for sync signals)
```

```
--
```

```
-- Horiz_sync  -----  
-- H_count      0                640                659                755                799  
--
```

```
IF (h_count = 799) THEN  
    h_count <= "0000000000";  
ELSE  
    h_count <= h_count + 1;  
END IF;
```

```
-- Generate Horizontal Sync Signal using H_count
```

```
if(h_count = 756) then  
    horiz_sync <= '1';  
end if;  
if(h_count = 659) then  
    horiz_sync <= '0';  
end if;
```

Video Signal Generator

```
--V_count counts rows of pixels (480 + extra time for sync signals)
--
--  Vert_sync      -----
--  V_count        0                480    493-494                524
--
IF (v_count = 524) AND (h_count = 799) THEN
    v_count <= "0000000000";
ELSIF (h_count = 799) THEN
    v_count <= v_count + 1;
END IF;
-- Generate Vertical Sync Signal using V_count
if (v_count = 493) then
    vert_sync <= '0';
end if;
if (v_count = 495) then
    vert_sync <= '1';
end if;
-- Generate Video on Screen Signals for Pixel Data
if(h_count = 639) then
    video_on_h <= '0';
end if;
if (h_count = 799) then
    video_on_h <= '1';
    if(v_count = 479) then
        video_on_v <= '0';
    end if;
    if(v_count = 524) then
        video_on_v <= '1';
    end if;
end if;
```

Video Signal Generator

```
-- Put all video signals through DFFs to eliminate
-- any logic delays that can cause a blurry image

red_out  <= red AND video_on;
green_out <= green AND video_on;
blue_out <= blue AND video_on;


END PROCESS;

END a;
```

Mouse Driver

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mousedriver is
  Generic( timeout: std_logic_vector(19 downto 0) := CONV_STD_LOGIC_VECTOR(100000,20));
  Port ( clock : in std_logic;
        reset : in std_logic;
        mouse_data : inout std_logic;
        mouse_clk : inout std_logic;
        left_button : out std_logic;
        right_button : out std_logic;
        mouse_cursor_row : out std_logic_vector(9 downto 0);
        mouse_cursor_column : out std_logic_vector(9 downto 0));
end mousedriver;
```

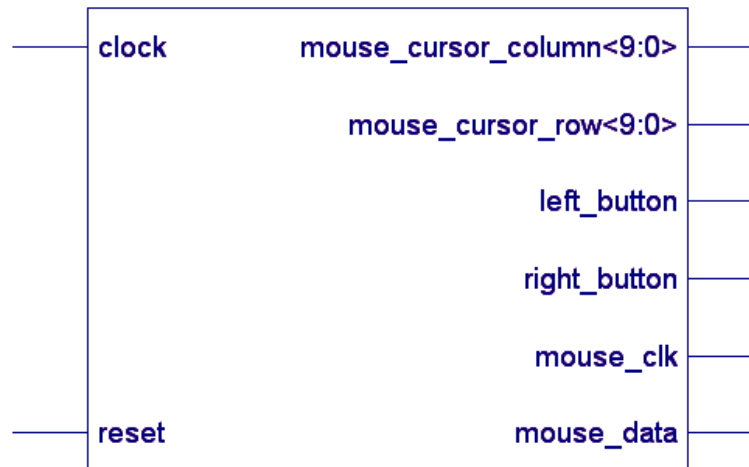

Mouse Driver

